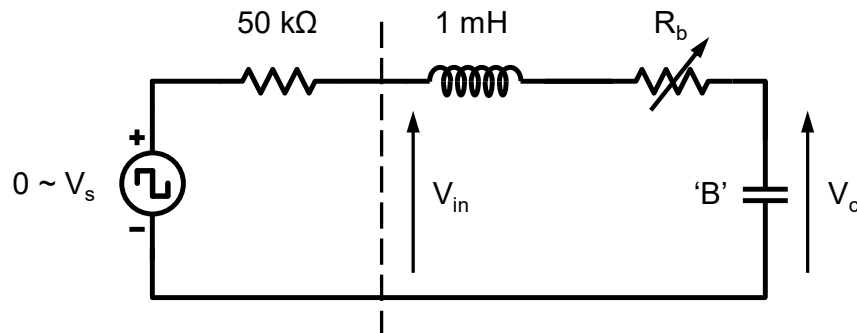


Question Statement:

Deduce (symbolic) expressions for α , ω , A and ϕ in terms of R , C , L and V_s for the circuit shown below, taking the initial charge on the capacitor when the square wave drops to zero volts to be CV_s and the current flowing at that time to be zero amps.



The governing equation for the L-C-R circuit is given as

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C}q = 0,$$

which is a linear, homogeneous, second-order ordinary differential equation. To derive the analytical solution to this equation, assume the solution are in the following form: $q(t) = e^{\lambda t}$, then the derivatives of q are $\frac{dq}{dt} = \lambda e^{\lambda t}$ and $\frac{d^2q}{dt^2} = \lambda^2 e^{\lambda t}$, respectively. Substituting these into the governing equation:

$$(\lambda^2 L + \lambda R + 1/C) e^{\lambda t} = 0,$$

yielding the auxiliary equation as $(\lambda^2 L + \lambda R + q/C) = 0$. Using the quadratic equation, the solutions of λ are given by

$$\lambda_{\pm} = \frac{-R \pm \sqrt{R^2 - \frac{4L}{C}}}{2L}.$$

To this end, one needs to discuss the sign of $R^2 - \frac{4L}{C}$, it eventually affects the form of general solution we will derive.

Case 1: $R^2 - \frac{4L}{C} < 0 \leftrightarrow R < 2\sqrt{\frac{L}{C}}$, there are two conjugate complex solutions of $\lambda = a \pm bi$, the solution of q will be in the form

$$q(t) = k_1 e^{\lambda_+ t} + k_2 e^{\lambda_- t} = k_1 e^{(a+bi)t} + k_2 e^{(a-bi)t} = e^{at} \cdot (k_1 e^{ibt} + k_2 e^{-ibt})$$

where $a = -\frac{R}{2L}$, $b = \frac{\sqrt{R^2 - \frac{4L}{C}}}{2L}$ are the real and imaginary parts of λ_{\pm} ; k_1, k_2 are constants yet to find. Expanding e^{ibt} and e^{-ibt} using Euler's formula:

Vibrations and Waves

$$e^{ibt} = \cos bt + i \sin bt$$

$$e^{-ibt} = \cos bt - i \sin bt$$

Substitute into the expression of $q(t)$ group sine terms and cosine terms:

$$\begin{aligned} q(t) &= e^{at} \cdot [k_1(\cos bt + i \sin bt) + k_2(\cos bt - i \sin bt)] \\ &= e^{at} \cdot [\underbrace{(k_1 + k_2)}_{\text{denote as } k_3} \cos bt + i \underbrace{(k_1 - k_2)}_{\text{denote as } k_4} \sin bt] \\ &= e^{at} \cdot [k_3 \cos bt + k_4 \sin bt]. \end{aligned}$$

Cf. the expression given out in the lab manual $q(t) = Ae^{-at} \cos(\omega t + \phi)$, we can deduce the following:

- $a = -\alpha$, hence $\alpha = \frac{R}{2L}$, which the rate of decay;
- $b = \omega = \frac{\sqrt{R^2 - \frac{4L}{C}}}{2L}$ which is the frequency of oscillation;
- k_3 and k_4 should be linked to A and ϕ ; the only way to achieve this is through the formula $\cos(a + b) = \cos(a)\cos(b) - \sin(a)\sin(b)$. As such, we deduce $k_3 = A \cos \phi$, $k_4 = A \sin \phi$. This is helpful, but still need to find the expression of A and ϕ using the known terms.

Apply the Dirichlet boundary condition: $q(0) = CV_s$ at $t = 0$, we know

$$A \cos \phi = CV_s$$

Apply the Neumann boundary condition: $i = \frac{dq}{dt} = 0$ at $t = 0$, we know

$$\frac{dq}{dt} = -A e^{-at} [\alpha \cos(\omega t + \phi) + \omega \sin(\omega t + \phi)],$$

hence,

$$\begin{aligned} \left. \frac{dq}{dt} \right|_{t=0} &= -\alpha A \cos \phi - \omega A \sin \phi = -\frac{R}{2L} \underbrace{CV_s}_{A \cos \phi} - \underbrace{\frac{\sqrt{R^2 - \frac{4L}{C}}}{2L}}_{\omega} A \sin \phi = 0 \\ \rightarrow A \sin \phi &= -\frac{RCV_s}{\sqrt{R^2 - \frac{4L}{C}}} \end{aligned}$$

Divide by $A \cos \phi = CV_s$:

$$\tan \phi = -\frac{R}{\sqrt{R^2 - \frac{4L}{C}}} \rightarrow \phi = \text{atan} - \frac{R}{\sqrt{R^2 - \frac{4L}{C}}}.$$

Having known the phase ϕ , the amplitude $A = \frac{CV_s}{\cos \phi}$.

Vibrations and Waves

Case 2: $R^2 - \frac{4L}{C} > 0 \leftrightarrow R > 2\sqrt{\frac{L}{C}}$, there are two real solutions of λ ; , the solution of q will be in the form

$$q(t) = k_1 e^{\lambda_+ t} + k_2 e^{\lambda_- t},$$

where $\lambda_{\pm} = \frac{-R \pm \sqrt{R^2 - \frac{4L}{C}}}{2L}$, k_1 and k_2 are constants subject to the boundary conditions.

Apply the Dirichlet boundary condition: $q(0) = CV_s$ at $t = 0$, we know

$$k_1 + k_2 = CV_s$$

Apply the Neumann boundary condition: $i = \frac{dq}{dt} = 0$ at $t = 0$, we know

$$\lambda_+ k_1 + \lambda_- k_2 = 0$$


Solving the simultaneous equations giving

$$k_1 = \frac{\lambda_- CV_s}{\lambda_+ - \lambda_-} = \frac{(-R - \sqrt{R^2 - \frac{4L}{C}}) \cdot CV_s}{2\sqrt{R^2 - \frac{4L}{C}}},$$

$$k_2 = \frac{\lambda_+ CV_s}{\lambda_+ - \lambda_-} = \frac{(-R + \sqrt{R^2 - \frac{4L}{C}}) \cdot CV_s}{2\sqrt{R^2 - \frac{4L}{C}}}.$$

Case 3: $R^2 - \frac{4L}{C} = 0$, derivation is neglected here as not required in the manual.


Mechanical equivalence:

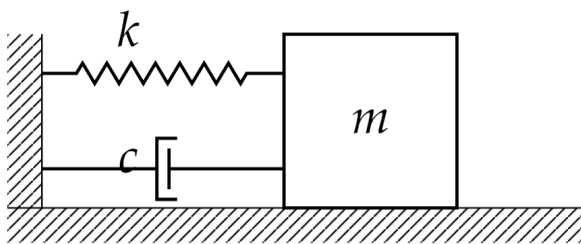

The same L-C-R circuit with the capacitor initially fully charged.

Question Statement:

By $\frac{V_c}{V_{in}} = \frac{1}{(1-\omega^2 LC) + j\omega CR}$, $\left| \frac{V_c}{V_{in}} \right|$ has a maximum when $\frac{d}{d\omega} \left(\left| \frac{V_c}{V_{in}} \right|^2 \right) = 0$, show that the resonance occurs at the frequency $\omega_{\text{peak}}^2 = \frac{1}{CL} - \frac{R^2}{2L^2}$.

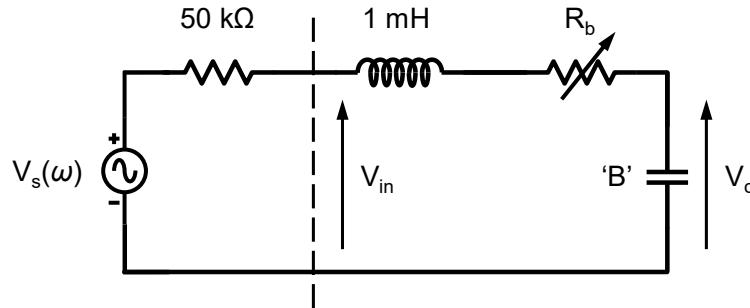

The magnitude of V_c/V_{in} is

$$\left| \frac{V_c}{V_{in}} \right| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega CR)^2}}$$

which reaches its maximum under the condition $\frac{d}{d\omega} \left(\left| \frac{V_c}{V_{in}} \right|^2 \right) = 0$, therefore,

$$\begin{aligned} \frac{d}{d\omega} \left| \frac{V_c}{V_{in}} \right|^2 &= \frac{d}{d\omega} \left(\frac{1}{1 + \omega^4 C^2 L^2 - 2\omega^2 CL + \omega^2 C^2 R^2} \right) \\ &= - \frac{4\omega^3 CL^2 - 4\omega CL + 2\omega C^2 R^2}{(1 + \omega^4 C^2 L^2 - 2\omega^2 CL + \omega^2 C^2 R^2)^2} \\ &= 0. \end{aligned}$$

Since the denominator cannot be zero, only the numerator will be zero:

$$4\omega^3 CL^2 - 4\omega CL + 2\omega C^2 R^2 = 0 \rightarrow \omega_{\text{peak}}^2 = \frac{1}{CL} - \frac{R^2}{2L^2}$$

For a small value of R , $\omega_{\text{peak}}^2 \approx \frac{1}{CL}$ since the term $\frac{R^2}{2L^2} \sim 0$. Substituting ω_{peak}^2 into $\left| \frac{V_c}{V_{in}} \right|^2$ yields

$$\left| \frac{V_c}{V_{in}} \right|_{\text{peak}}^2 = \frac{1}{\left(1 - \frac{1}{CL} \cdot LC\right)^2 + \left(\frac{1}{CL} \cdot C^2 R^2\right)} = \frac{L}{CR} \rightarrow \left| \frac{V_c}{V_{in}} \right|_{\text{peak}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$