



# BIOE40002 – Computer Fundamentals and Programming 1


*Part I – Digital Logics, Lab 2*


*Binghuan Webster Li | Department of Bioengineering*

*[binghuan.li19@imperial.ac.uk](mailto:binghuan.li19@imperial.ac.uk)*

**January 27, 2022**

# Meme of the day...

 

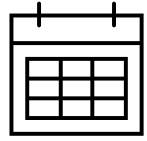

# Today's Schedule

- Recap (~ 10 mins)
  - From decimal to binary, binary addition
  - Half adders
  - Full adders
  - From 2-bit adders to 4-bit adders – increase of the bit
- Live demonstration of Quartus Prime Lite
- Lab exercises 6 & 7
- Quiz time!

# 1010 From decimal to binary

Example: convert  $(11)_{10}$  into the binary form

- Step 1: strip down  $(11)_{10}$  into the sum of  $2^n$   
 $11 = 1 + 2 + 8 = 2^0 + 2^1 + 2^3$
- Step 2: express each presented term in 0 or 1

	$2^3$	$2^2$	$2^1$	$2^0$
Presented?	YES	NO	YES	YES
Binary	1	0	1	1

- Therefore,  $(11)_{10} = (1101)_2$

To convert decimal to binary:

$$a_n \cdot 2^n + \dots + a_1 \cdot 2^1 + a_0 \cdot 2^0$$

# Binary addition

Example: perform addition  $(11)_{10} + (7)_{10}$  in binary


$$\begin{array}{r}
 (11)_{10} \qquad \qquad 1 \ 0 \ 1 \ 1 \\
 (7)_{10} \qquad \qquad \quad 0 \ 1 \ 1 \ 1 \\
 \hline
 (11)_{10} + (7)_{10} \quad \begin{array}{c} \color{gray}{1} \ \color{gray}{1} \ \color{gray}{1} \ \color{gray}{1} \\ \color{blue}{1} \ 0 \ 0 \ 1 \ 0 \end{array} \\
 \hline
 \text{carry (C) out} \quad \text{sum (S)}
 \end{array}$$

Verify:

$$(11)_{10} + (7)_{10} = \mathbf{18} = (10010)_2$$
 
# Half adders

- Q: How to use logic gates to perform binary additions?
- A: Start with 2-bit addition: **a half adder**



<i>A</i>	<i>B</i>	<i>C</i>	<i>S</i>
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	0


**Half** –No *carry-in* from the previous step (column) can be taken in. It can only stick to the 2-bit additions!

$$\begin{array}{r}
 (1)_{10} \qquad \qquad \qquad 0 \ 1 \\
 (3)_{10} \qquad \qquad \qquad \underline{1 \ 1} \\
 (1)_{10} + (3)_{10} \qquad \qquad 1 \ 0 \ 0
 \end{array}$$


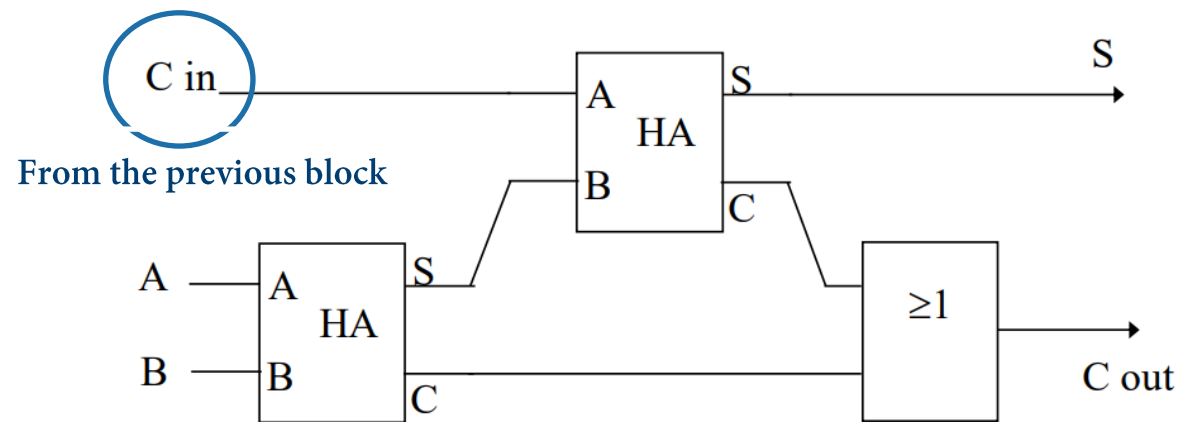
# Full adders

- **Q:** What if we want to perform additions with the carry-in from the previous steps?
- **A:** try with an intermediate adder !




<i>A</i>	<i>B</i>	<i>C<sub>in</sub></i>	<i>S</i>	<i>C<sub>out</sub></i>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Take a closer look to  $C_{in}$ : carry (out) from the last bit (see next slide)
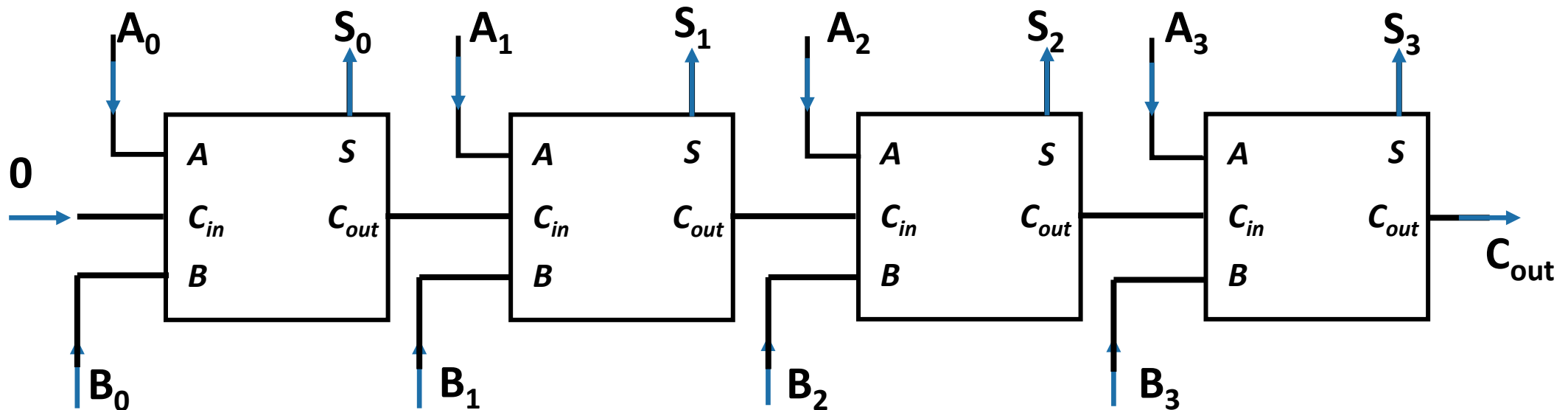
# Increase the bit

- In the last 2 slides, we have seen the use of adders for 2-bit additions.
- To increase the bit, we can achieve this by simply connecting full-adders together.



- A 4-bit adder – can evaluate e.g. 1010 + 0011



*Questions?*

# Using Quartus Prime Lite v16.0

- License are required for Quartus Prime Lite users.
- Why bother? Use college standard set-ups in the [Software Hub](#)
  - Need a college [VPN](#) to use the Software Hub on your own PC –A bit laggy...?
  - [Remote connection](#) to your college account!
- Two versions are available in the Software Hub
  - V 16.0 and V 20.0, very similar features
  - **Go for v16.0!**




*Questions ?*


*That's it for now.*

*You can now proceed to the Exercise 6 and 7.*
 
# Task 6 – Design a half-adder with *NAND* gates





A	B	C	S
1	1	1	0
1	0	0	1
0	1	0	1
0	0	0	0

 


- Grid size = 10ns
- end time = 1us
  
# Task 7 – Design a full adder

- design a full adder with two half adders and an OR gate



- Grid size = 10ns
- end time = 1us

 

## Quiz Time!

- Q1 – One day, when you are having your beef jagga at JCR, a post-doc at EEE comes to you and says that he wants to build some adders. You know he has some real troubles as he was graduated from UCL. As a smart Bioeng student, can you help him to identify which of the following statement(s) regarding adders is/are NOT true?
  - a) A half adder is constructed with a XOR gate and an OR gate*
  - b) A full adder is better than half adder as it has a carry out output*
  - c) A full adder can do multi bit binary addition*
  - d) A full adder is a combinational logic circuit*

- Q2 – The next week, the post-doc brings you a 4-bit addition circuit which is assembled by himself. However, the circuit does not work at all. You decide to help him debug. First, you compile a check-list. Which of the following statement(s) from the check-list should be true about a 4-bit addition machine?
  - a) It requires 4 full adders*
  - b) It requires 5 full adders*
  - c) The carry in of the full adder corresponding to the most significant bit is connected to the carry out of the full adder corresponding to the second most significant bit*
  - d) The carry out of the full adder corresponding to the most significant bit is connected to the carry in of the full adder corresponding to the second most significant bit*
  - e) None of the above is true*