



BIOE40002 – Computer Fundamentals and Programming 1


Part I – Digital Logics, Lab 5

Binghuan Webster Li | Department of Bioengineering


binghuan.li19@imperial.ac.uk

February 17, 2022

Meme of the day...

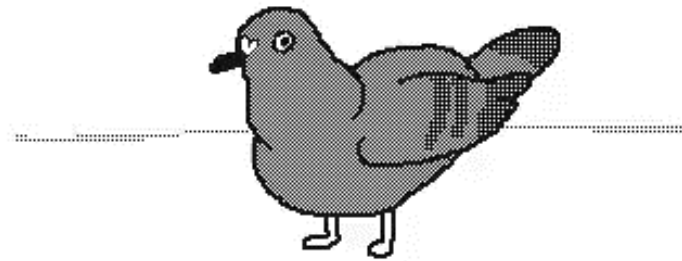

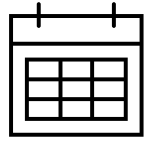When your program is a complete mess, but it does it's job.



Today's Schedule


- Recap (~ 10 mins)
 - Integration of the 4-bit addition and subtraction machine
 - Selectors and multiplexers
- Lab exercises 11 and 12

4-bit addition and subtraction machine


- *Q*: can we integrate addition and subtraction functions into *one* machine?
- *Rationale*: a condition to determine whether inverting the input bits is required!

$C_{in} = 0$,
addition

$C_{in} = 1$,
subtraction

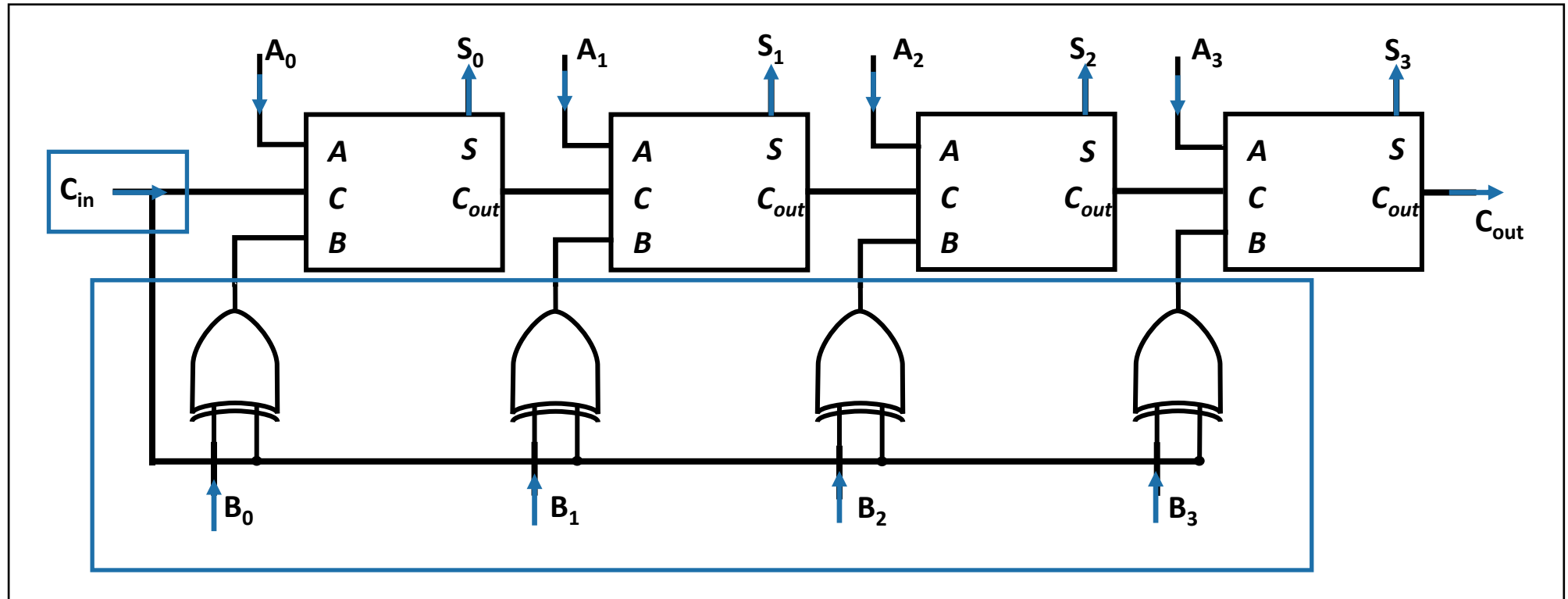


AND gates as selectors

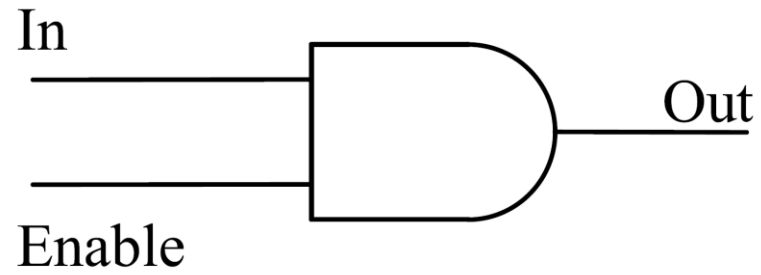


<i>Enable</i>	<i>In</i>	<i>Out</i>
0	0	0
0	1	0
1	0	0
1	1	1

- When *Enable* is set to 1, output follows input
- When *Enable* is set to 0, output would remain 0 regardless of the value of input
- Selector

2 × 1 multiplexer

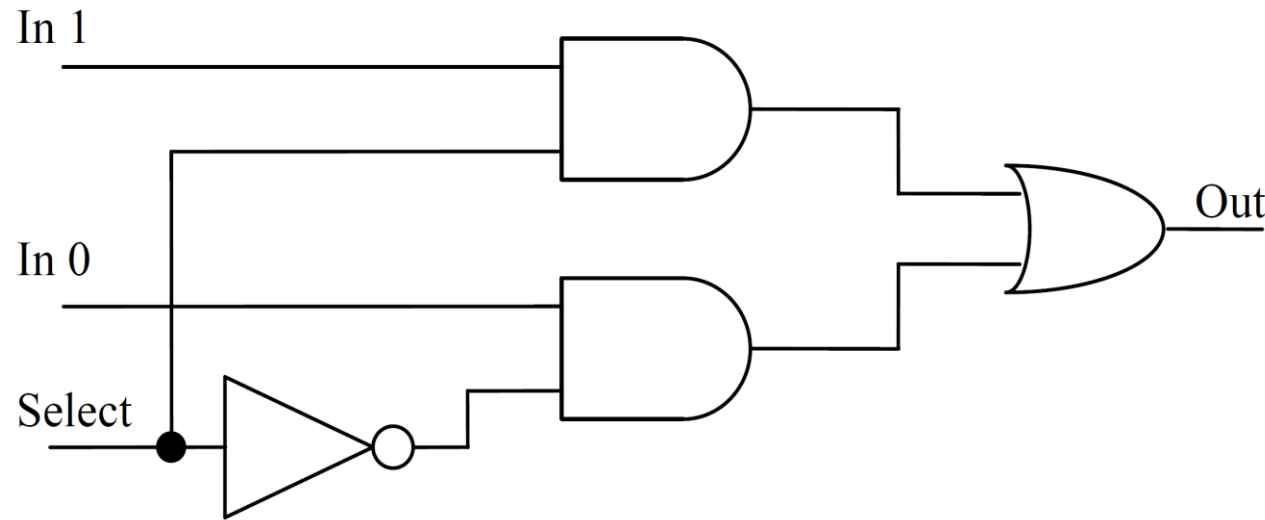


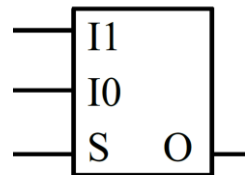- When *Select* is set to 1, output follows input channel 1 (*In1*)
- When *Select* is set to 0, output follows input channel 0 (*In0*)
- 2 × 1 multiplexer



<i>In 0</i>	<i>In 1</i>	<i>Select</i>	<i>Out</i>
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

4 × 1 multiplexer

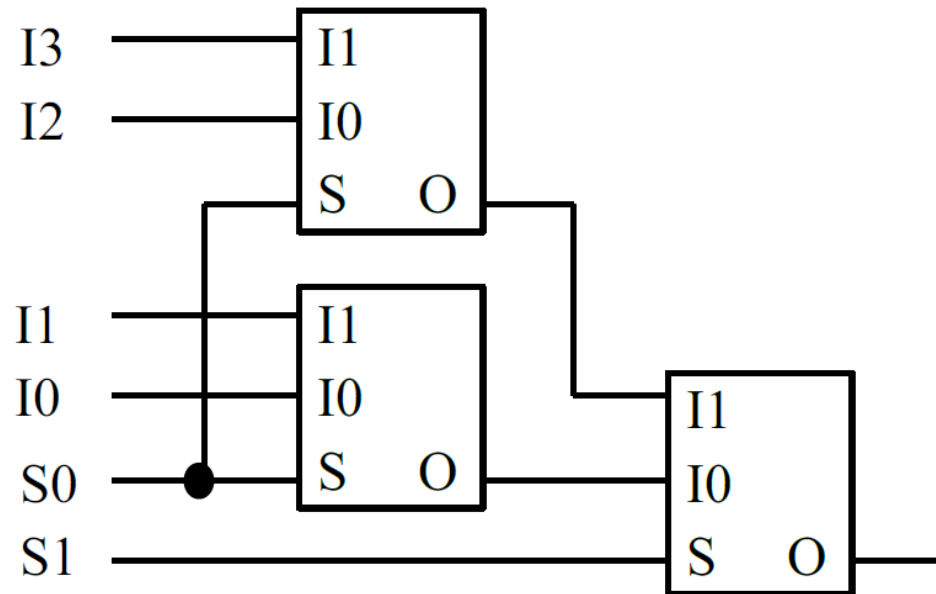

- 2 selector terminals – S_0, S_1
- Select the signal from I_0, I_1, I_2, I_3
- E.g., $S_0=1, S_1=1; O=I_3$


It is your turn to design a 8×1 multiplexer with two 4×1 multiplexers and one 2×1 multiplexer!

Questions?

That's it for now.

You can now proceed to the Exercise 10 and 11.

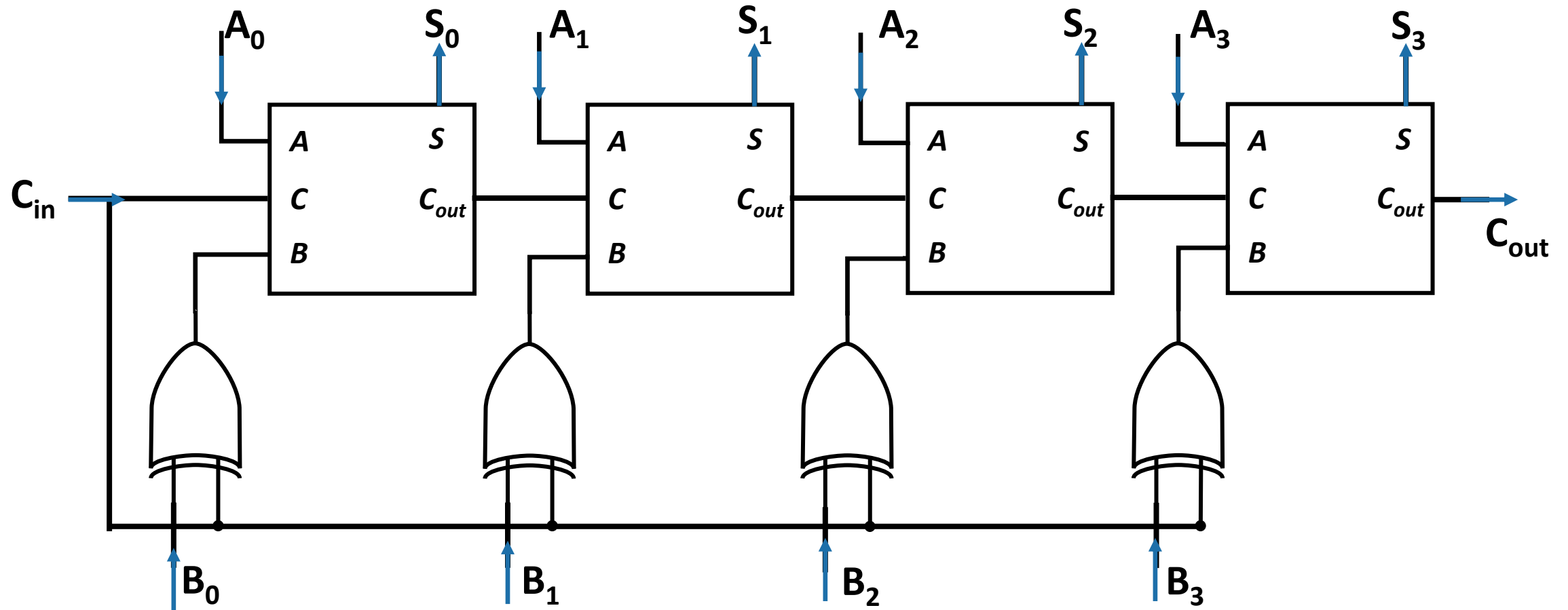Task 11 – design a 4-bit add-subtraction circuit



- By setting $C_{in} = 0$, the circuit performs addition
- By setting $C_{in} = 1$, the circuit performs subtraction

Task 12 – Design an 8x1 multiplexer

